

## Node Voltage Method (Nodal Analysis)

The Node Voltage Method, also referred to as Nodal Analysis, is the systematic application of KCL to solve for the voltages across each circuit element.

### Definitions:

**Node (N):** An electrical juncture connecting two or more circuit elements.

**Essential Node (EN):** An electrical juncture connecting three or more circuit elements.

**Reference Node (gnd):** An essential node referenced to zero volts or ground.

**Super Node (SN):** A composite node comprising two or more ENs connected by a paths containing only independent and/or a dependent voltage sources.

### Nodal Analysis:

1. Identify and label all the Essential Nodes - assume there are “n” ENs.
2. Choose and label one EN as the reference node - call this reference node ground (zero Volts).
3. Identify and label all Super Nodes - assume SNs consists “m” ENs.
4. Generate one KCL equation for each EN excluding the reference node and any EN which is part of a SN.
5. Generate one KCL equation for each SN which does not contain the reference node.
6. Generate “m-1” constraint equations for each SN in terms of the voltages at the ENs.
7. Generate one constraint equation for each dependent voltage source and dependent current source in terms of the voltages at the ENs - assume there are “d” dependent sources.
8. This process will generate a linear system of “d+n-1” equations with “d+n-1” unknowns. Solve the system of equations to determine the voltages at the ENs and the values of the dependent sources.
9. Use the calculated values of the voltages from step 8 to solve for the voltages across and the current through each circuit element.