## ECE 210 Exam #3 = 5 Apr. | 2013

#1 
$$i_2R_2 + 40 \frac{di_2}{dt} + 16 e^{-400t} = 0$$

$$N_1(t) = 10 \frac{di_3(t)}{dt} + 5 \frac{di_2}{dt} = 32 e^{-400t} + 5 \frac{di_2}{dt}$$

#2 
$$\lambda_1(0^+) = 5.64A$$
  
 $\lambda_1(\infty) = 10.5A$   
 $\lambda_1(t) = 10.5 - 4.86e^{-6wot}$ 

#3 
$$N_1(0^-) = -20V$$
  $N_2(0^-) = 0V$ 
 $N_1(0^+) = 0V$   $N_2(0^+) = 0V$ 
 $N_1(5y_5) = -1.212V$   $N_2(5y_5) = 0V$ 
 $N_1(15y_5) = -2.92V$   $N_2(15y_5) = -32.92V$ 

## ECE 209 Exam #3 - 25 November 2014

#1 
$$\hat{L}_{2}(0^{-}) = 0$$
 A
$$\hat{L}_{2}(0^{+}) = 0$$
 A
$$\hat{L}_{3}(0^{+}) = 0$$
 A
$$\hat{L}_{4}(0^{+}) = 0$$
 A
$$\hat{L}_{5}(0^{+}) = 0$$
 A
$$\hat$$

#2 
$$\lambda_1(0^-) = 0A$$
  $\lambda_1(0^+) = 0.467A$ 
 $\lambda_2(0^-) = 0.583A$   $\lambda_2(0^+) = 0.583A$ 
 $\lambda_3(0^-) = 0.117A$   $\lambda_3(0^+) = 0A$ 
 $N_L(0^-) = 0V$   $N_L(0^+) = 7V$ 
 $N_3(0^-) = 7V$   $N_3(0^+) = 0V$ 

#3 
$$V_c(t) = S(1 - e^{-40(t - SX10^{-3})}) V$$

$$V_R(t) = Se^{-40(t - SX10^{-3})} V$$

# 4 
$$V = 4 (45^{\circ} V)$$
 $T = 25 (-10^{\circ} A)$ 
 $N(t) = 6 (05 (19,000 Ti t + 40^{\circ}) V$ 
 $L(t) = 21 \cos (10,000 Ti t + 65^{\circ}) A$ 
 $6.414 + j1.414$  or  $6.57 (12.43^{\circ})$ 
 $3.42 + j9.40$  or  $10 (-70^{\circ})$ 
 $12 - j32$  or  $34.18 (-69.44^{\circ})$ 

## ECE 209 Exam #3 = 3 April 2015

#2 T= 0.526 MS T= 30ms

#3 
$$\lambda_{c}(0^{-}) = 0 A$$
  $\lambda_{c}(0^{+}) = 6.75 \text{mA}$   $\lambda_{c}(\infty) = 0$ 

$$\lambda_{c}(0^{-}) = 1 \text{mA} \quad \lambda_{c}(0^{+}) = -0.688 \text{mA} \quad \lambda_{c}(\infty) = 1 \text{mA}$$

$$N_{c}(0^{-}) = -120 \text{V} \quad N_{c}(0^{+}) = -120 \text{V} \quad N_{c}(\infty) = 150 \text{V}$$

$$N_{c}(0^{-}) = 150 \text{V} \quad N_{c}(0^{+}) = -103.1 \text{V} \quad N_{c}(\infty) = 150 \text{V}$$

## ECE 209 Exam #4 - 22 April 2015

#1 2.5V

2 m S

1.77V

2.5 cos (1000 TI t - 600) V

V= 15 (200 mV

I = 25 (-250 A

N(t)= 12 (05 (50,001 Tt -400) V

i (t) = 2 (05 (50,000 iit + 650) A

6.414-j1.586 or 6.607 (-13.89°

1.389+j7-878 or 8/800