

ECE 209 — Exam # 3

Estimated time for completion: <75 minutes
22 November 2016

Rules of the Exam

Rule 1: The examination period begins at 11:00pm on Tuesday 24 November 2015 and ends at 12:15pm on Tuesday 24 November 2015.

Rule 2: There are three problems.

Rule 3: Show all work and state all assumptions. Make sure to include the units along with a numerical answer. Answers without support when needed will not receive credit.

Rule 4: The exam is closed book and closed notes. You may have an 8.5" x 11" sheet of paper with notes. You may use a calculator.

Answer Key


Name



Happy Thanksgiving!

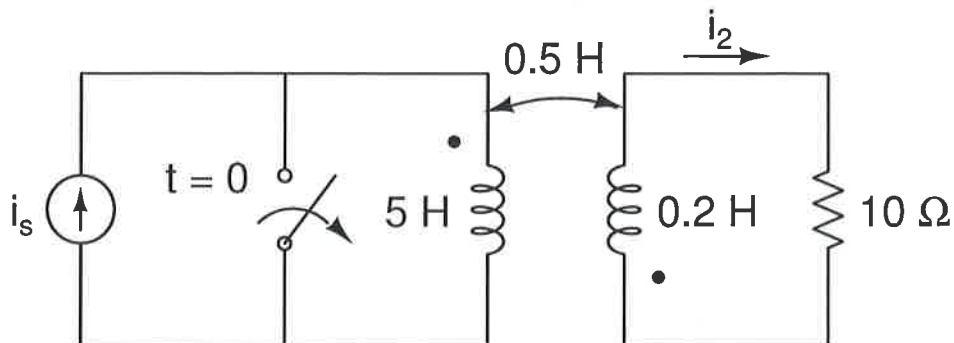Problem 1 (20 points)

In the circuit below, the switch has been closed for a very long time and opens at $t = 0$. There is no energy stored in the circuit at the time the switch opens.



What is $i_2(0^-)$ 0 A


What is $i_2(0^+)$ 0 A

What is the differential equation that describes the behavior of $i_2(t)$ for $t \geq 0$? (Note: you do not need to solve the equation.)

$$10i_2 + 0.2 \frac{di_2}{dt} + 0.5 \frac{di_s}{dt} = 0$$

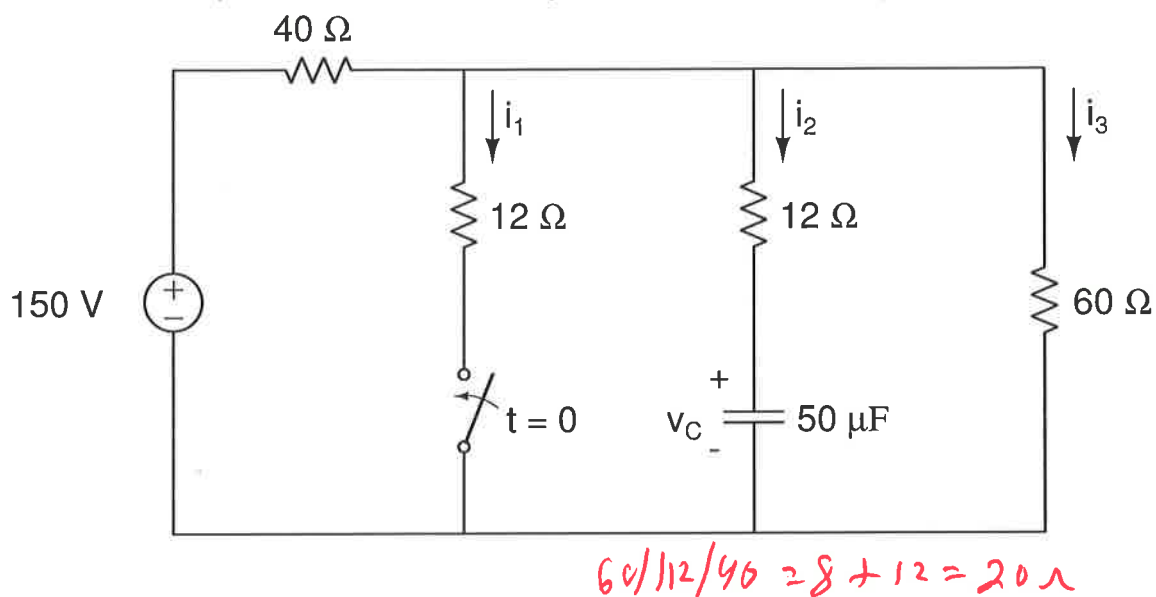Problem 2 (40 points)

In the circuit below, the switch has been open for a very long time and closes at $t = 0$.



What is the time constant of the circuit for $t > 0$? 1 ms
RC


See Page 6

Complete the table below:

	$t = 0^-$	$t = 0^+$	$t = 4 \text{ ms}$	$t = \infty$
i_1	0 A	4.5 A	2.54 A	2.5 A
i_2	0 A	-3.0	-0.055 A	0 A
i_3	1.5 A	0.9 A	0.507 A	0.5 A
v_C	90 V	90 V	31.1 V	30 V

Problem 3 (40 points)

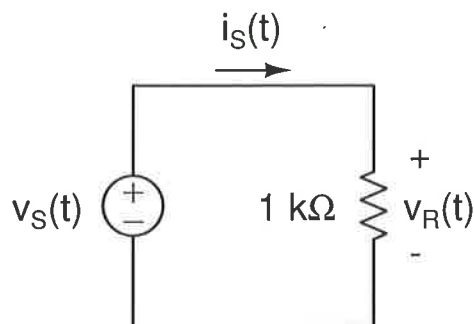Part A. For the circuit below the voltage source $v_s(t) = 150 \cos(2513t - 55^\circ)$ V



What is the peak voltage across the resistor?

150 V

What is $v_s(4\text{ms})$?

-141.77 V

What is $i_s(4\text{ms})$?

-141.77 mA

What is the frequency of $v_R(t)$ in Hz?

400 Hz

What is the average power dissipated by the resistor?

11.25 W

Part B. What is the Phasor representation of the following time-domain signals?

$$v(t) = 120 \cos(360t - 37^\circ) \text{ mV}$$

$120 \angle -37^\circ \text{ mV}$

$$i(t) = 75 \sin(450t + 40^\circ) \text{ A}$$

$75 \angle -50^\circ \text{ A}$

Part C. What is the time-domain representation of the following Phasor signals when the frequency is 3 MHz?



$$\mathbf{V} = 25 \angle -50^\circ \text{ V}$$

$25 \cos(6\pi \times 10^6 t - 50^\circ) \text{ V}$

$$\mathbf{I} = 0.3 \angle 15^\circ \text{ A}$$

$0.3 \cos(6\pi \times 10^6 t + 15^\circ) \text{ A}$

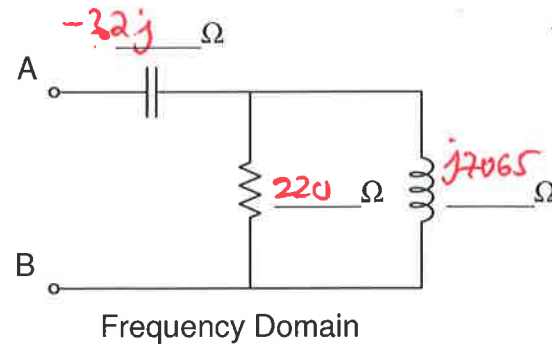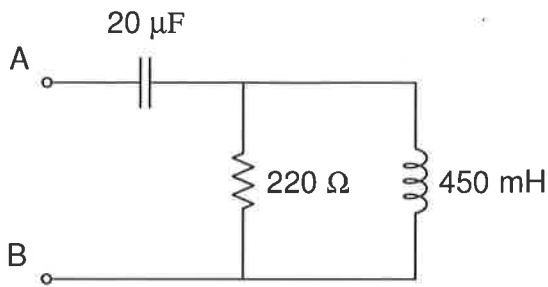Part D. Convert the circuit below on the left to the frequency domain when the frequency is 2.5 kHz.



At what radian frequency, ω , is the impedance Z_{AB} purely resistive? 333.3 rad/s

$$Z_{AB} = -\frac{j}{\omega C} + \frac{220 \times j\omega L}{220 + j\omega L}$$

$$= -\frac{j}{\omega C} + \frac{220 j\omega L (220 - j\omega L)}{220^2 + \omega^2 L^2}$$

$$\text{Im}(Z_{AB}) = -\frac{j}{\omega C} + \frac{(220)^2 j\omega L}{(220)^2 + \omega^2 L^2} = 0$$

$$\Rightarrow -(220)^2 + (\omega^2 L^2) + (220)^2 \omega^2 LC = 0$$

$$\omega^2 (220^2 LC - L^2) = 220^2$$

$$\omega^2 (220^2 LC - L^2) = 220^2$$

$$-\frac{j}{\omega C} + R \frac{j\omega L}{R + j\omega L}$$

$$-\frac{j}{\omega C} + \frac{j\omega LR}{R + j\omega L} \frac{R - j\omega L}{R - j\omega L}$$

$$-\frac{j}{\omega C} + \frac{j\omega LR^2 + \omega^2 L^2 R}{R^2 + \omega^2 L^2}$$


$$-\frac{1}{\omega C} + \frac{\omega LR^2}{R^2 + \omega^2 L^2} = 0$$

$$-R^2 - \omega^2 L^2 + \omega^2 LC R^2 = 0$$

$$\omega^2 (LC R^2 - L^2) = R^2$$

$$\omega^2 = \frac{R^2}{(LC R^2 - L^2)}$$
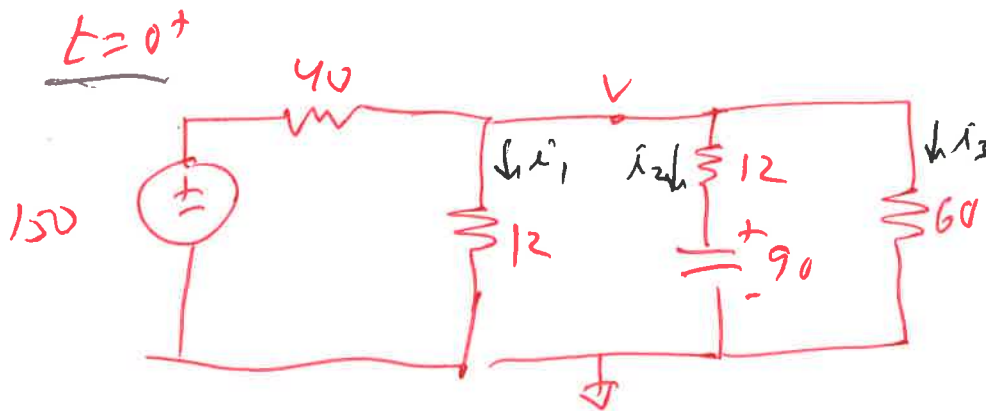
$$\omega = \frac{220}{\sqrt{220^2 LC - L^2}} = 333.3 \text{ rad/s}$$



$$\frac{V-150}{40} + \frac{V}{12} + \frac{V}{60} + \frac{V-90}{12} = 0$$

$$V = 54V$$

$$i_1 = 2.5 + [4.5 - 2.5]e^{-t} = 2.537 \text{ A}$$

$$i_2 = -3e^{-t} = -0.055 \text{ A}$$

$$i_3 = 0.5 + [0.9 - 0.5]e^{-t} = 0.507 \text{ A}$$

$$V_c = 30 + 60e^{-t} = 31.1 \text{ V}$$

Name: _____