

## ECE 209 — Exam # 3

Estimated time for completion: <1.25 hour  
21 November 2017

### Rules of the Exam

**Rule 1:** The examination begins at 9:30am on Tuesday 21 November 2017 and ends at 10:45pm on Tuesday 21 November 2017.

**Rule 2:** There are three problems.

**Rule 3:** The exam is closed book and closed notes. You may use an 8.5" x 11" sheet of paper with notes and a calculator.

**Rule 4:** Do not leave the room until you have completed the exam.

**Rule 5:** To receive full credit for an answer include the units along with the numerical answer.


**Rule 6:** Show all work - answers without supporting work will not receive credit.

Answer Key

\_\_\_\_\_  
Name

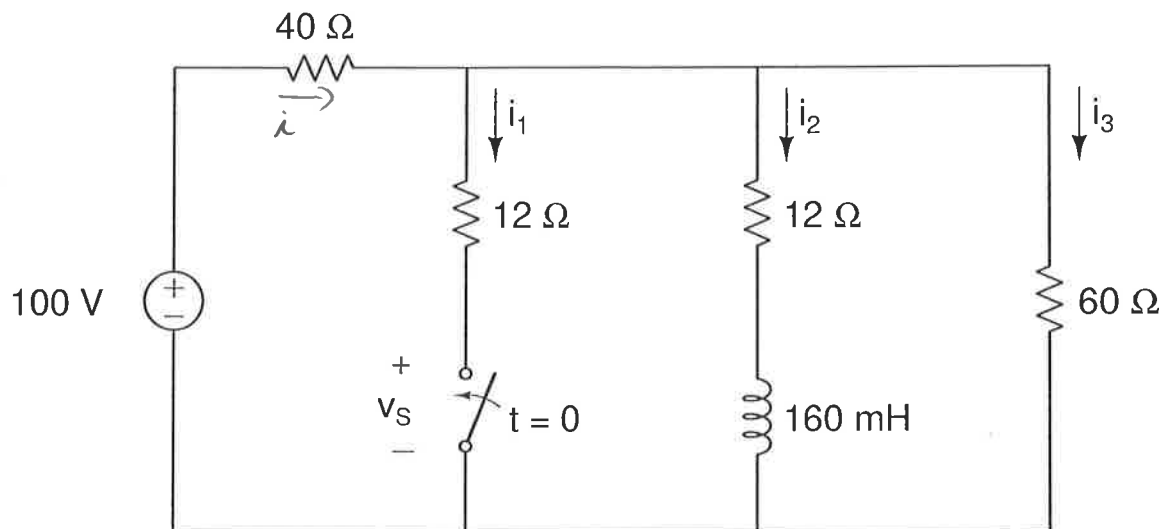**Problem 1** (30 points)

In the circuit below, the switch has been open for a very long time, and closes at  $t = 0$ .



$$\tau = \frac{L}{R}$$

$$R = 40 \parallel 12 \parallel 60 + 12 = 20 \Omega$$

$$12 \parallel 60 = 10$$

$$12 \parallel 12 \parallel 60 = 5.45$$

What is the time constant of the circuit for  $t > 0$ ?  $\tau = 8 \text{ ms}$


$$t = \infty \quad i = 2.2 \text{ A}$$

Complete the table below: *See page 5.*

	$t = 0^-$	$t = 0^+$	$t = 10 \text{ ms}$	$t = \infty$
$i_1$	0 A	0.553 A	0.872 A	1.0 A
$i_2$	1.67 A	→ 1.67 A	1.192 A	1.0 A
$i_3$	0.33 A	0.111 A	0.775 A	0.2 A
$v_S$	20 V	0 V	0 V	0 V

Problem 2 (40 points)

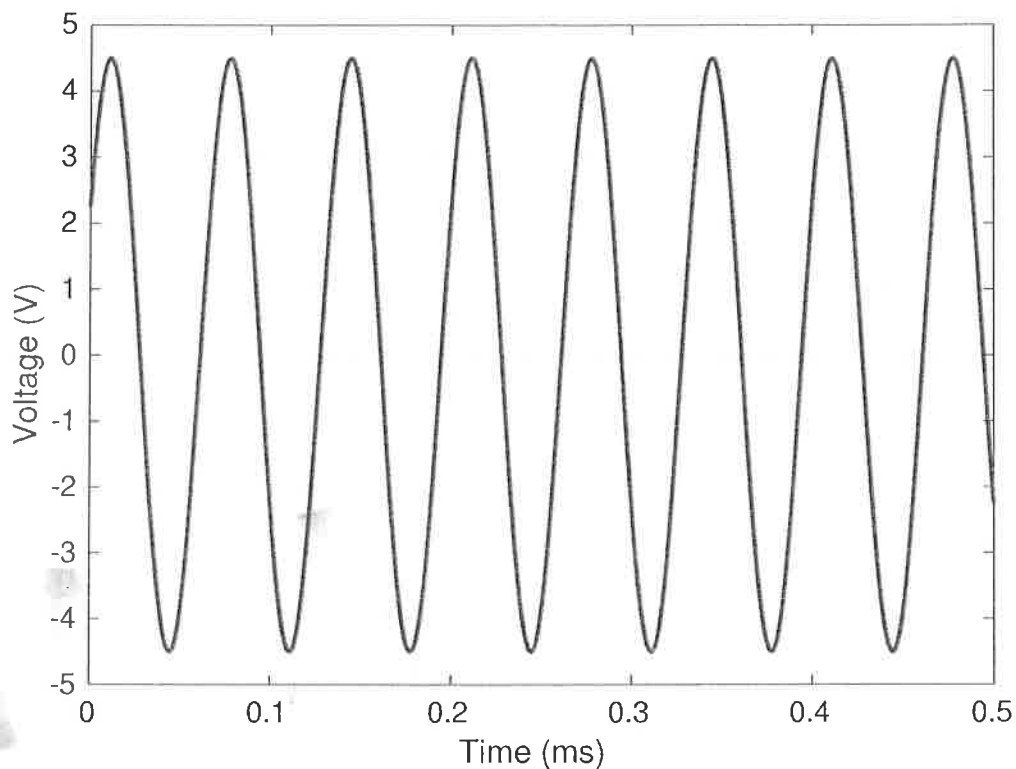Part A: Consider the voltage waveform shown below:



What is  $V_{RMS}$ ?

3.18 V

What is the peak-to-peak voltage?

9.0 V

What is the frequency in Hz?

15 KHz

What is the equation for  $v(t)$ ?

$4.5 \cos(30 \times 10^3 \pi t - 60^\circ)$

What is  $\mathbf{V}$  the Phasor representation of  $v(t)$

$4.5 \angle -60^\circ$

**Problem 3** (30 points)

Perform the following operations. Express your result in either rectangular (Cartesian) or polar notation.



$$2\angle 60^\circ - 4j =$$

$$\underline{1 - j2.27 \text{ or } 2.48\angle -66.2^\circ}$$

$$(4\angle 40^\circ \times 2\angle 40^\circ) + (8 + j8) =$$

$$\underline{9.39 + j15.9 \text{ or } 18.45\angle 59.4^\circ}$$

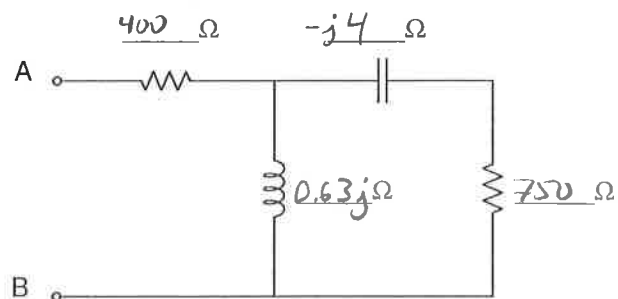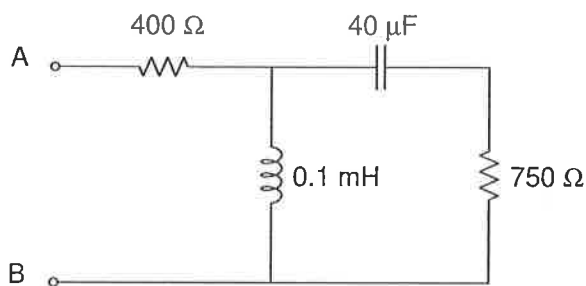Convert the circuit on the left to the frequency domain when the frequency is 1 kHz.



What is the equivalent impedance between terminals A and B?  $400 + 0.63j$


$$Z_{AB} = (750 - j4) \parallel (0.63j) + 400$$

$$\left( \frac{1}{750 - j4} + \frac{1}{j0.63} \right)^{-1} + 400$$

$$5.3 \times 10^{-4} + 0.63j$$

(Blank Page)

@  $t = 0^+$

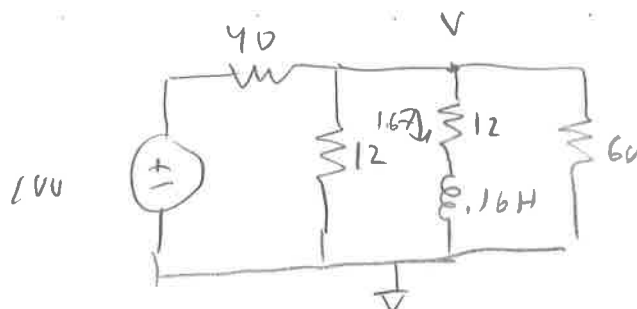

$$\text{KCL @ } V: \frac{V}{60} + 1.67 + \frac{V}{12} + \frac{V - 100}{40} = 0$$

$$V = 6.64V$$

(Blank Page)